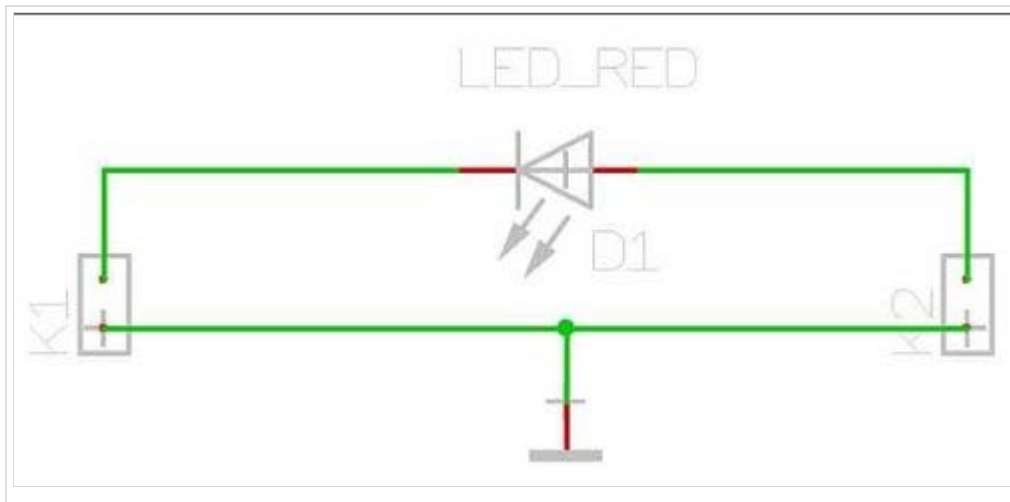


Simulate the function Part 1


From IBF-Wiki


This article is part of an introduction tutorial called CrashCourse2
Download this article as PDF-File

The simulation in TARGET 3001! is a matter of the schematic. So we switch over to it and see our well known picture:





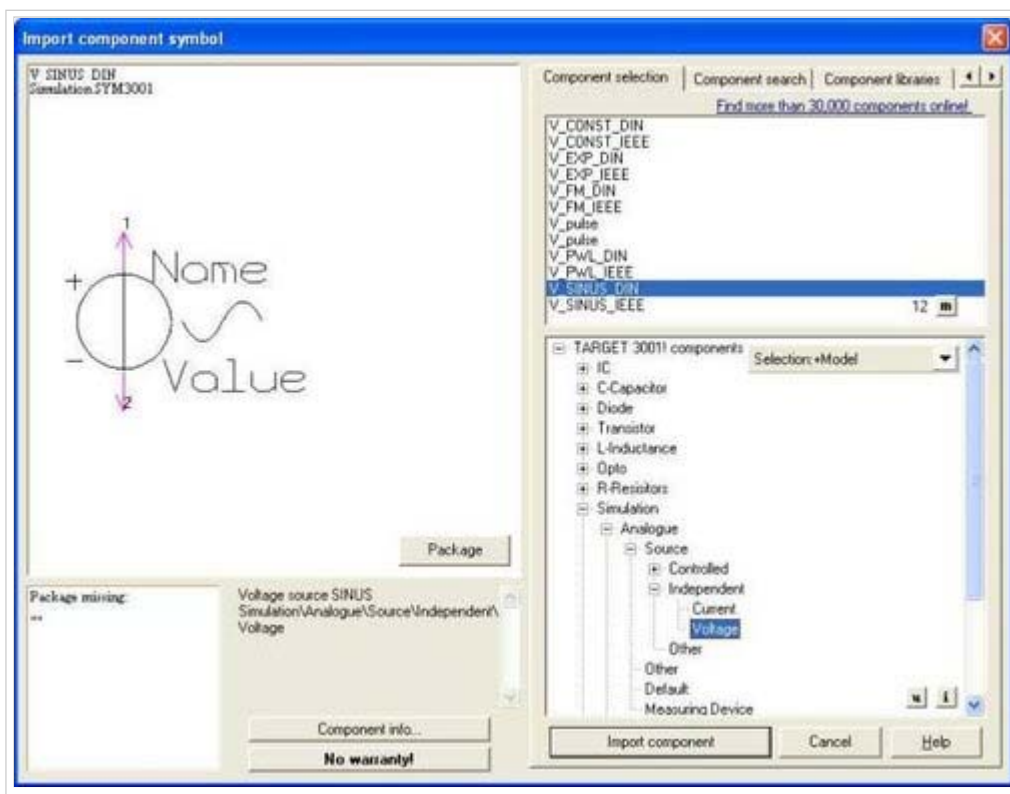For the simulation of the LED's function we need a voltage source, and a load resistance. Those components will not be part of the layout thus don't have a package. Find such components in the tree view in the branch **Simulation**. First we import a sinus - source, then a resistor.




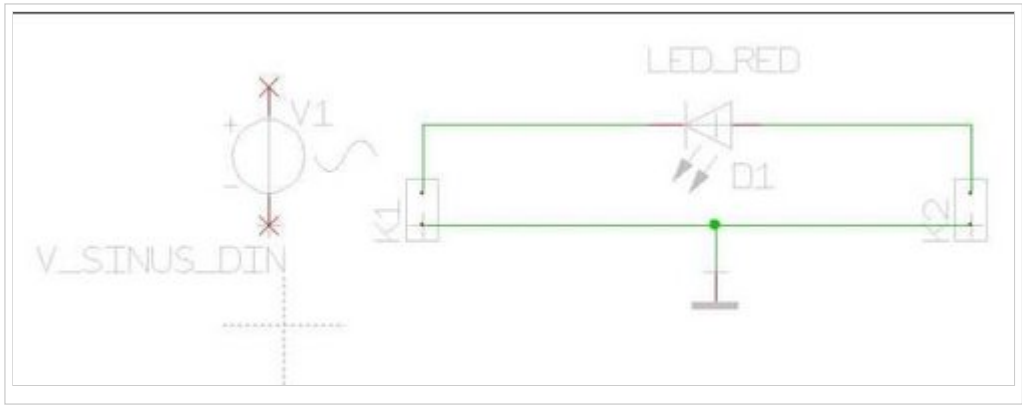

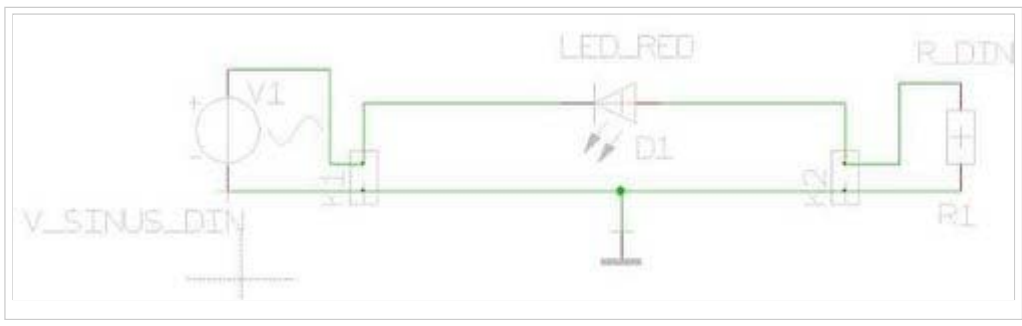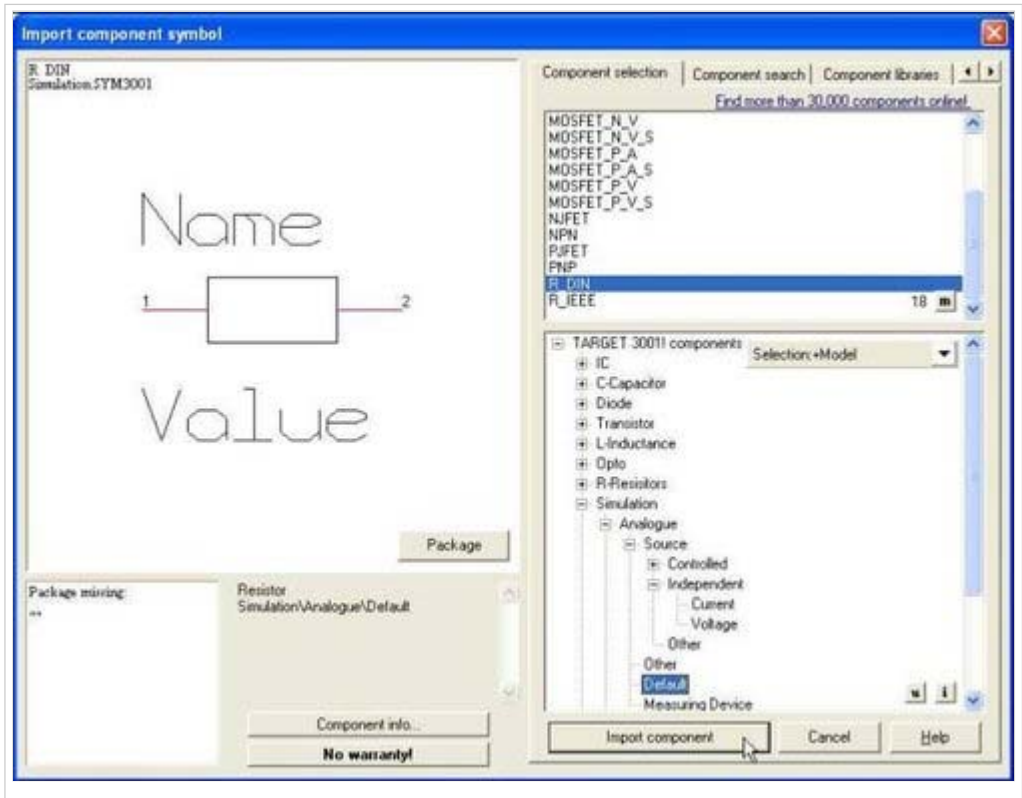
The resistor we pick from the branch Simulation/Analogue/Source/Default and connect it accordingly:



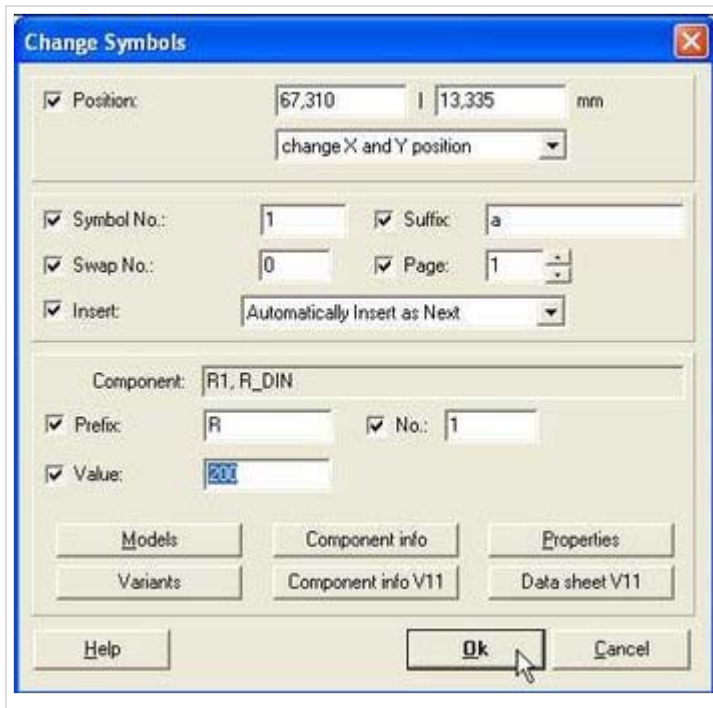
Now we set the values for source and load, first **M11** on the handle cross of the resistor:



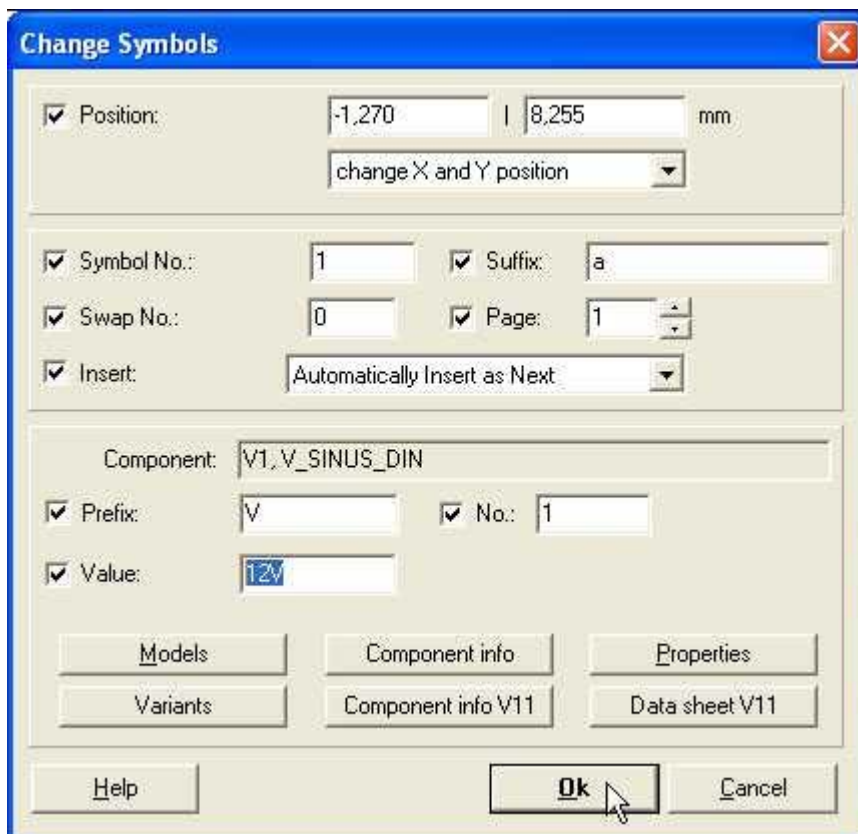
Now we enter component value "200", this stands for 200 Ohm. Press OK. Now press **M11** upon the handle cross of the sinus source:



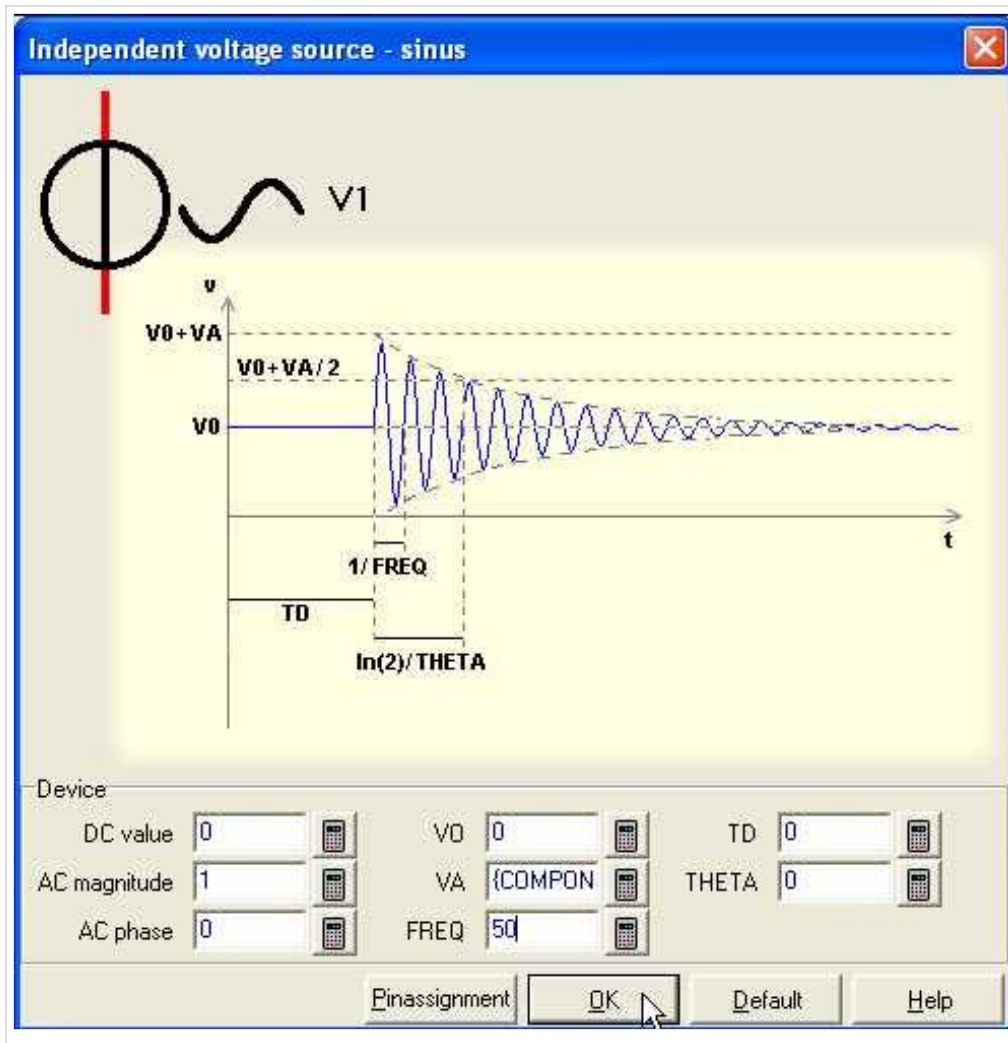We define its component value by 12V. By the use of the "Models" button in the same dialog we set the frequency. In the following dialog press button "Edit". Afterwards a setting of the parameters can be done:



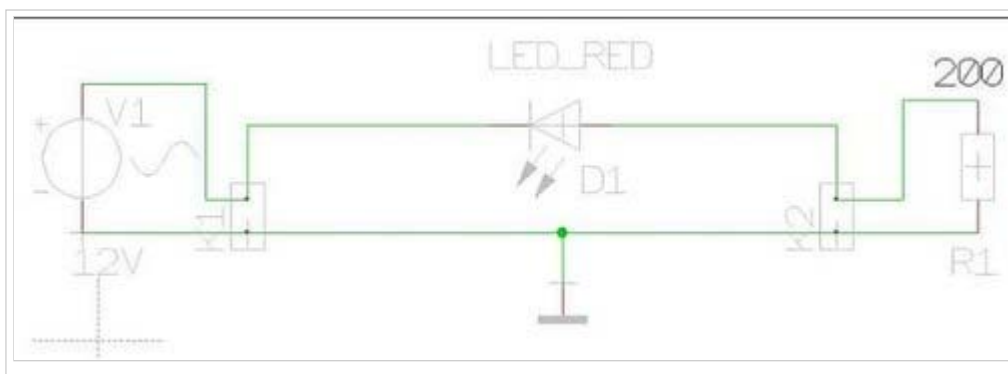At "FREQ" enter value 50. Now the preliminaries are done. We confirm all dialogs and the schematic might look like this:



Next step
One Step back

Back to the overview

Retrieved from "http://server.ibfriedrich.com/wiki/ibfwikien/index.php?title=Simulate_the_function_Part_1"

Categories: Simulation

IBF-Intern:

- This page was last modified 13:57, 15 January 2009.
- This page has been accessed 4,053 times.